

การออกแบบคิช - คิช ก่อน เวอร์ เคอร์



นายพันธุ์ เพพ เลาห์บ

วิทยานิพนธ์นี้ เป็นส่วนหนึ่งของการศึกษาทางหลักสูตรปริญญา

วิศวกรรมศาสตร์มหาบัณฑิต

แผนกวิศวกรรมไฟฟ้า

นักวิเคราะห์ฯ ทุ่งกรรณมหาวิทยาลัย

พ.ศ. 2516

002001

I16656751

OPTIMUM DESIGN OF DC - DC CONVERTER

Mr. Panthep Laochachai

A Thesis Submitted in Partial Fulfillment of the

Requirements for the Degree of Master of

Engineering

Department of Electrical Engineering

Graduate School

Chulalongkorn University

1973

บัณฑิตวิทยาลัย จุฬาลงกรณ์มหาวิทยาลัย อนุมติให้เน้นวิทยานิพนธ์ฉบับ<sup>๑</sup>  
นี้เป็นส่วนหนึ่งของการศึกษาตามหลักสูตรปริญญามหาบัณฑิต

นาย สมชาย.

คณบดีบัณฑิตวิทยาลัย

คณะกรรมการครุยวิทยานิพนธ์

นาย ไชยรัตน์.

ประธานกรรมการ

ดร. มนต์รัตน์.

กรรมการ

ดร. ไสวรัตน์.

กรรมการ

อาจารย์ผู้ควบคุมการวิจัย นางรุ่งนันท์ มังคละวิริยะ

ที่ว่าด้วยวิทยานิพนธ์ การออกแบบคึชี - คึชี คณเวอร์ เกอร์  
 จืด นายพันธุ์ เพพ เลาห์ย  
 แผนกวิศวกรรมไฟฟ้า  
 ปีการศึกษา พ.ศ. 2515



นพดล

วิทยานิพนธ์ฉบับนี้มีรูปมุ่งหมายเพื่อศึกษาหาวิธีออกแบบ คึชี - คึชี คณเวอร์ เกอร์ ที่สามารถจ่ายกำลังไฟฟ้าตามที่ต้องการได้ โดยมีประสิทธิภาพสูงแก่มีขนาดเล็ก การวิจัยนี้เริ่มจากการออกแบบ คณเวอร์ เกอร์ที่ให้กำลังไฟฟ้าและข้อกำหนดต่าง ๆ กัน ขั้นตอนไปเป็นการวิจัยสาเหตุที่ทำให้เกิดการสูญเสียกำลัง หาวิธีที่ทำให้เกิดการสูญเสียกำลังน้อยที่สุด และหาวิธี เลือกอุปกรณ์ที่มีขนาดเล็กแต่ใช้ได้ดี ขั้นสุดท้ายเป็นการสรุปหลักการและวิธีออกแบบคณเวอร์ เกอร์ เป็นความลักษณะ ภาระวิจัยที่ทำให้การออกแบบคณเวอร์ เกอร์ ได้ผลเป็นที่พอใจ ซึ่งจะเป็นประโยชน์ต่อการสร้างงานจรรยาดังไฟฟ้าสำหรับงานจริย์เล็กในนิคส์ก่อไป.

Thesis Title    Optimum Design of DC - DC Converter

Name              Mr. Panthep Laochachai

Department of Electrical Engineering

Academic Year 1972

#### ABSTRACT

The purpose of this research is to obtain practical procedures in designing a dc - dc converter which possesses a compact size and at the same time could produce high **power** efficiency in power conversion. The first step of this study is to design converters of various specifications. Then the power losses in each component are analysed and the optimum values of parameters and components are investigated. Finally, the design procedure and component selection criterions are summarized. As a result the design dc - dc converters of small size, light weight with high efficiency of operation can be achieved.

#### ACKNOWLEDGEMENTS

The author is highly indebted to Mr. Virul Mangclaviraj for his valuable advice in preparing this research work. Special thanks are to the Office of Atomic Energy for Peace for permission to use the research room's facilities. Also thanks to Mr. Supot Promnaret for his help solving an equation by computer.

To all those people, named and unnamed and those who have encouraged him in the research, his very sincere thanks.

## CONTENTS

TITLE	PAGE
ABSTRACT ( THAI )	iv
ABSTRACT ( ENGLISH )	v
ACKNOWLEDGEMENT	vi
CONTENTS	vii
LIST OF FIGURES AND TABLE	viii
LIST OF SYMBOLS	x
CHAPTER	PAGE
1 INTRODUCTION	1
2 TYPES OF CONVERTER	3
3 DESIGN CRITERIONS	5
4 DESIGN PROCEDURE	12
5 DESIGN SAMPLES	16
6 DERIVATION OF THE FORMULAE	24
7 ILLUSTRATIONS	30
8 DISCUSSION	47
9 CONCLUSION AND RECOMMENDATION	49
REFERENCES	50
VITA	51

## LIST OF FIGURES AND TABLE

Figure		Page
1	Self-oscillating converter .....	30
2	Driven converter .....	30
3	Waveforms of self- oscillating converter .....	31
4	Some other self-oscillating converter circuits .....	32
5	Driver circuit for the converter .....	33
6	Waveforms of the 15W, 25-100V, self-oscillating converter	33
	6-A Base to emitter voltage .....	34
	6-B Collector to emitter voltage.....	34
	6-C Feedback voltage .....	35
	6-D Base current .....	35
	6-E Collector current .....	36
	6-F Collector current at no load .....	36
	6-G $I_C$ and $V_{CE}$ during switching ON .....	37
	6-H $I_C$ and $V_{CE}$ during switching OFF .....	37
	6-I Transformer primary voltage .....	38
	6-J Transformer secondary voltage .....	38
7	Waveforms of the 15W, 25-100V, driven converter	
	7-A Base current .....	39
	7-B Collector current .....	39
	7-C Collector to emitter voltage .....	40
	7-D $V_{CE}$ when the frequency is less than 3.3 kHz .....	40
	7-E $I_C$ when the frequency is less than 3.3 kHz .....	41
8	B-H curve of TDK, H5B, ferrite core .....	41
9	Circuit for determining B-H curve .....	42

10	Operating characteristics of the 15W, 25-100V self-oscillating converter .....	43
11	Efficiency v.s. frequency curve of the 15W, 25-100V driven converter .....	44
12	Operating characteristics of the 15W, 25-100V driven converter .....	45
13	Feedback Voltage Table .....	46



## LIST OF SYMBOLS

- $A_{\text{core}}$  ... core cross sectional area (  $\text{cm}^2$  )  
 $B_{\text{max}}$  ... maximum magnetic flux density ( gauss )  
 $B_{\text{sat}}$  ... saturated magnetic flux density ( gauss )  
 $f$  ..... frequency ( Hz )  
 $h_{\text{FE}}$  ..... dc current gain of a transistor  
 $I_B$  ..... base current ( A )  
 $I_C$  ..... collector current ( A )  
 $I_{\text{in}}$  ..... input current ( A )  
 $I_{\text{out}}$  ..... output current ( A )  
 $J$  ..... current density (  $\text{A}/\text{cm}^2$  )  
 $K_w$  ..... a factor used in determining maximum power handling of a core  
 $K_l$  ..... a factor to compensate for transformer voltage drop and losses  
 $l_w$  ..... mean length of one turn of conductor wire ( cm )  
 $N_1$  ..... primary turn  
 $N_2$  ..... secondary turn  
 $N_{\text{FB}}$  ..... feedback turn  
 $n$  ..... allowable fraction of voltage drop in wire  
 $P_{\text{in}}$  ..... input power ( watt )  
 $P_{\text{out}}$  ..... output power ( watt )  
 $P_h$  ..... hysteresis loss ( watt )  
 $P_{\text{max}}$  ..... maximum power handling by a core ( watt )  
 $R_1$  ..... base-bias resistance ( ohm )  
 $R_2$  ..... base-bias resistance ( ohm )  
 $V$  ..... volume of a core (  $\text{cm}^3$  )

- $V_{CE(sat)}$  ..... collector to emitter saturation voltage ( v )  
 $V_{BE(sat)}$  ..... base to emitter saturation voltage ( v )  
 $V_{FB}$  ..... feedback voltage ( v )  
 $V_{in}$  ..... input voltage ( v )  
 $V_{out}$  ..... output voltage ( v )  
 $v_d$  ..... voltage drop in a coil ( v )  
 $V_B$  ..... bias voltage ( v )  
 $w$  ..... window area of a core (  $\text{cm}^2$  )  
 $\rho$  ..... resistivity ( ohm-cm )  
 $\eta$  ..... efficiency  
 $\phi$  ..... magnetic flux ( weber )